

**DIGITAL DESIGN**

**CS223**

**LAB-02 PRELIMINARY REPORT**

---

**NAME: MUHAMMAD ARHAM KHAN**

**BILKENT ID: 21701848**

**SECTION: 2**

**DATE: 23 Oct, 2018**

**TRAINING PACK: 47**


# 1-BIT FULL ADDER

## BOOLEAN EQUATION:

$$\text{SUM} = (X \text{ XOR } Y) \text{ XOR } C_{\text{IN}}$$

$$C_{\text{OUT}} = ((X \text{ XOR } Y) \cdot C_{\text{IN}}) + (X \cdot Y)$$

## CIRCUIT SCHEMATIC:

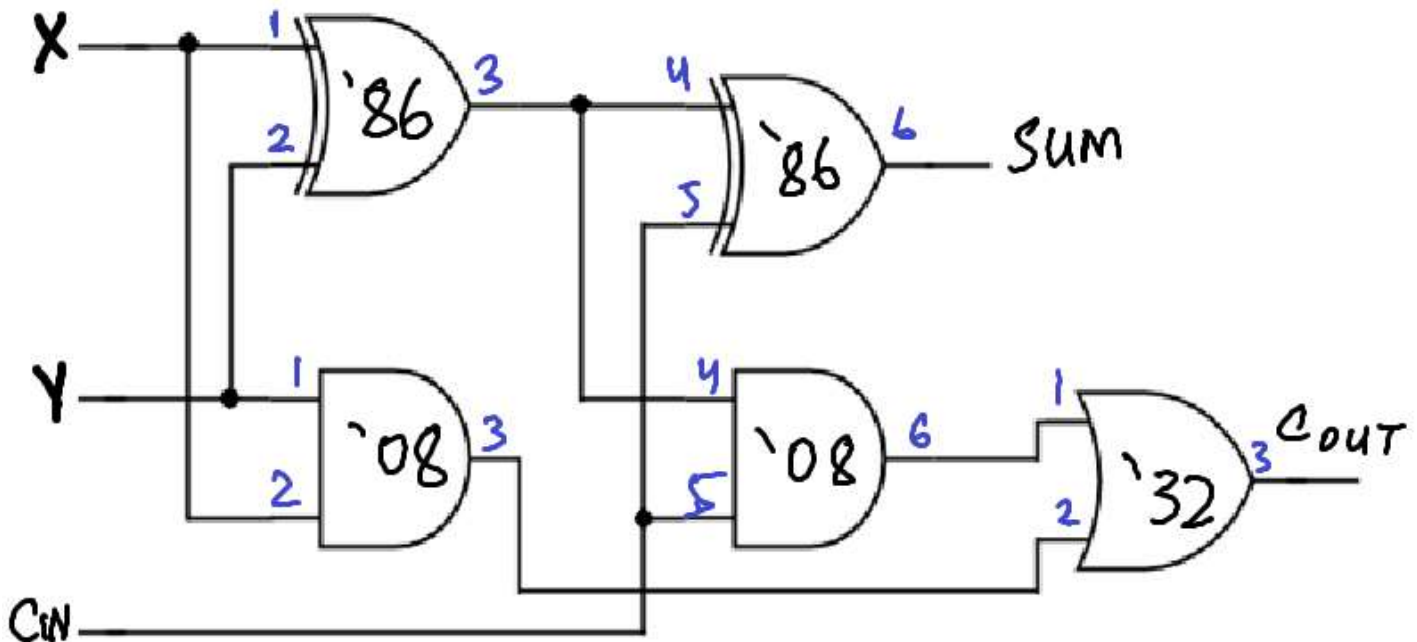

7486  
GND-7  
+5V-14

7408  
GND-7  
+5V-14


7432  
GND-7  
+5V-14

## IC LIST:


- ONE 7408 QUAD 2-INPUT AND GATE
- ONE 7486 QUAD 2-INPUT XOR GATE
- ONE 7432 QUAD 2-INPUT OR GATE

# 2-BIT ADDER

## LOGIC DIAGRAM (BLACK-BOXED):

 

## CIRCUIT SCHEMATIC:

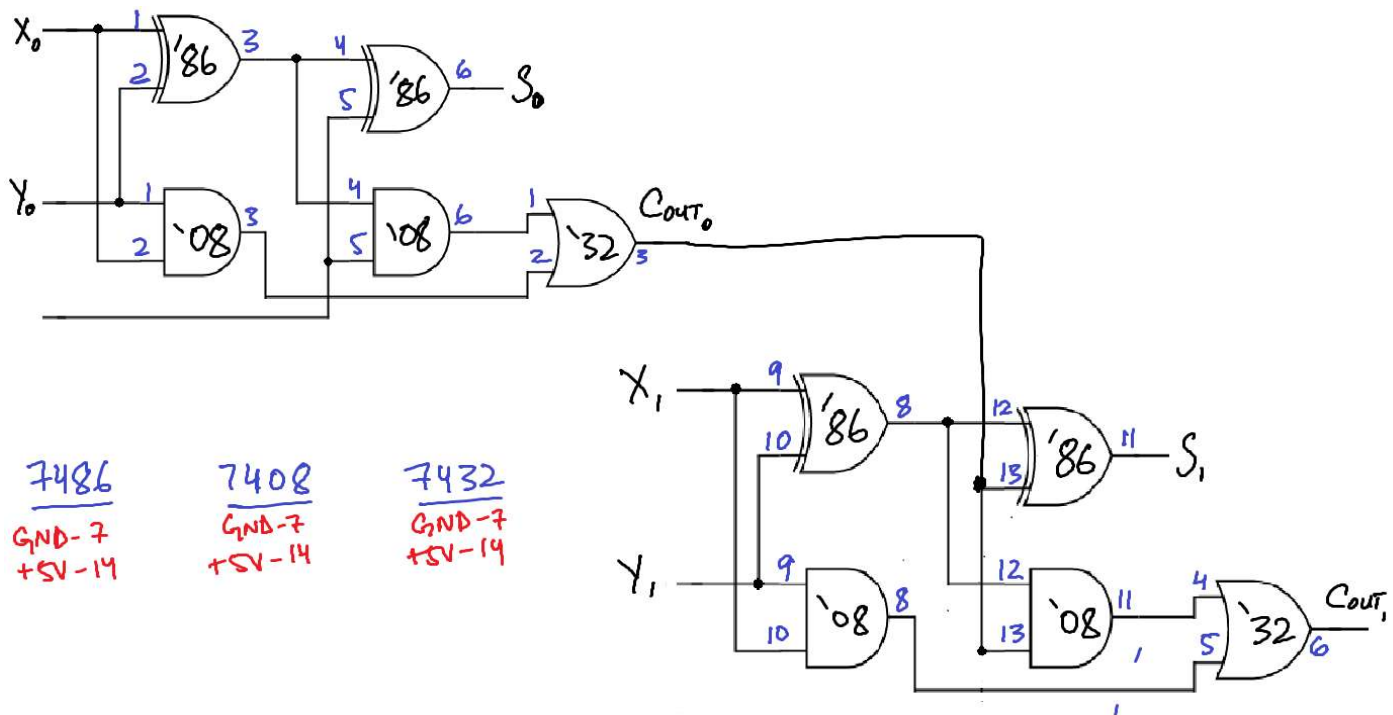

## IC LIST:

- ONE 7408 QUAD 2-INPUT AND GATE
- ONE 7486 QUAD 2-INPUT XOR GATE
- ONE 7432 QUAD 2-INPUT OR GATE

**1-BIT FULL ADDER DATAFLOW(BEHAVORIAL) SYSTEMVERILOG MODULES**

```

module oneBitFullAdder( input logic x, y, cin
    Output logic s, cout);

    logic p, g;

    assign p=x^y;
    assign g=x&y;

    assign s=p^cin;
    assign cout=g | (p & cin);
endmodule

```

**TESTBENCH:**

```

module oneBitFullAdder_testb();
    logic x, y, cin, s, cout;

    //instantiate the device in testbench
    oneBitFullAdder dut( x, y, cin, s, cout);

    //start applying inputs( one by one)
    initial begin
        x=0; y=0; cin=0; #10;
        cin=1; #10;
        y=1; cin=0; #10;
        cin=1; #10;
        x=1; y=0; cin=0; #10;
        cin=1; #10;
        y=1; cin=0; #10;
        cin=1; #10;
    end
endmodule

```

# 1-BIT FULL ADDER STRUCTURAL SYSTEMVERILOG MODULES

```

module oneBitFullAdder( input logic x, y, cin
                        Output logic s, cout);

    logic a, b, c;

    xor( a, x, y);
    and( b, x, y);
    xor( s, a, cin);
    and( c, a, cin);
    or( cout, b, c);
endmodule

```

## TESTBENCH:

```

module oneBitFullAdder_testb();
    logic x, y, cin, s, cout;

    //instantiate the device in testbench
    oneBitFullAdder dut( x, y, cin, s, cout);

    //start applying inputs( one by one)
    initial begin
        x=0; y=0; cin=0; #10;
        cin=1; #10;
        y=1; cin=0; #10;
        cin=1; #10;
        x=1; y=0; cin=0; #10;
        cin=1; #10;
        y=1; cin=0; #10;
        cin=1; #10;
    end
endmodule

```

## 2-BIT ADDER STRUCTURAL SYSTEMVERILOG MODULES

```

module twoBitAdder( input logic[1:0] x, y ,
                    input logic cin0,
                    output logic[1:0] s,
                    output logic cout1);

    logic cout0;

    oneBitFullAdder( x[0], y[0], cin0, s[0], cout0);
    oneBitFullAdder( x[1], y[1], cout0, s[1], cout1);
endmodule

```

### TESTBENCH:

```

module twoBitAdder_testb();
    logic[1:0] x, y, s;
    logic cin0, cout1;

    //instantiate the device in testbench
    twoBitAdder dut( x, y, cin0, s, cout1);

    //start applying inputs( one by one)
    initial begin
        x[0]=0; x[1]=0; y[0]=0; y[1]=0; cin0=0; #10;
        cin0=1; #10;
        y[1]=1; cin0=0; #10;
        cin0=1; #10;
        y[0]=1; y[1]=0; cin0=0; #10;
        cin0=1; #10;
        y[1]=1; cin0=0; #10;
        cin0=1; #10;
        x[1]=1; y[0]=0; y[1]=0; cin0=0; #10;
        cin0=1; #10;
    end

```

```
y[1]=1; cin0=0; #10;
cin0=1; #10;
y[0]=1; y[1]=0; cin0=0; #10;
cin0=1; #10;
y[1]=1; cin0=0; #10;
cin0=1; #10;
x[0]=1; x[1]=0; y[0]=0; y[1]=0; cin0=0; #10;
cin0=1; #10;
y[1]=1; cin0=0; #10;
cin0=1; #10;
y[0]=1; y[1]=0; cin0=0; #10;
cin0=1; #10;
y[1]=1; cin0=0; #10;
cin0=1; #10;
x[1]=1; y[0]=0; y[1]=0; cin0=0; #10;
cin0=1; #10;
y[1]=1; cin0=0; #10;
cin0=1; #10;
y[0]=1; y[1]=0; cin0=0; #10;
cin0=1; #10;
y[1]=1; cin0=0; #10;
cin0=1; #10;
```

end

endmodule