

**DIGITAL DESIGN**

**CS223**

**LAB-04 PRELIMINARY REPORT**

---

**NAME: MUHAMMAD ARHAM KHAN**

**BILKENT ID: 21701848**


**SECTION: 2**

**DATE: 26 NOV, 2018**

**TRAINING PACK: 47**

# MOORE FINITE STATE MACHINE (FSM)

## TRANSITION DIAGRAM

 

## STATE ENCODINGS

STATE	ENCODING $S_{2:0}$		
	$S_2$	$S_1$	$S_0$
S0	0	0	0
S1	0	0	1
S2	0	1	0
S3	0	1	1
S4	1	0	0
S5	1	0	1
S6	1	1	0
S7	1	1	1

## OUTPUT ENCODING

OUTPUT	ENCODING	
	$L_1$	$L_0$
RED	0	0
YELLOW	0	1
GREEN	1	0

## OUTPUT TABLE

STATE	$L_A$		$L_B$	
	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
S0	1	0	0	0
S1	0	1	0	0
S2	0	0	0	0
S3	0	0	0	1
S4	0	0	1	0
S5	0	0	0	1
S6	0	0	0	0
S7	0	1	0	0

# STATE TRANSITION TABLE

CURRENT STATE			INPUTS		NEXT STATE		
$S_2$	$S_1$	$S_0$	$T_A$	$T_B$	$S_2$	$S_1$	$S_0$
0	0	0	1	X	0	0	0
0	0	0	0	X	0	0	1
0	0	1	X	X	0	1	0
0	1	0	X	X	0	1	1
0	1	1	X	X	1	0	0
1	0	0	X	1	1	0	0
1	0	0	X	0	1	0	1
1	0	1	X	X	1	1	0
1	1	0	X	X	1	1	1
1	1	1	X	X	0	0	0

## NEXT STATE EQUATIONS

$$S_0' = (S_2 + S_1 + T_A) \cdot (S_1 + \overline{S_2} + T_B) \cdot S_0$$

$$S_1' = S_1 \overline{S_0} + \overline{S_1} S_0$$

$$S_2' = S_2 \overline{S_1} + S_2 \overline{S_0} + S_1 S_0 \overline{S_2}$$

## OUTPUT EQUATIONS


$$L_{A0} = \overline{S_2} \overline{S_1} S_0 + S_2 S_1 S_0$$

$$L_{A1} = \overline{S_2} \overline{S_1} \overline{S_0}$$

$$L_{B0} = \overline{S_2} S_1 S_0 + S_2 \overline{S_1} S_0$$

$$L_{B1} = S_2 \overline{S_1} \overline{S_0}$$


# FSM CIRCUIT SCHEMATIC

 

## HOW MANY FLIP-FLOPS ARE NEEDED?

Since there are total 8 states and using the binary encoding, we have three bits used to store the 8 states, we will need to use 3 Flip-Flops for the implementation.

## DETAILED CIRCUIT DESIGN

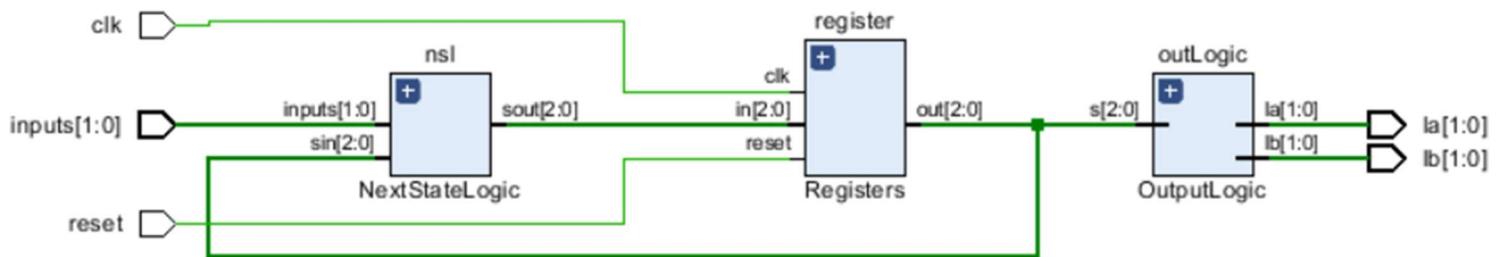

# TRAFFIC LIGHTS (SYSTEM VERILOG)

```

module TrafficLights( input logic clk, reset,
                    input logic[1:0] inputs,
                    output logic[1:0] la, lb);

    logic[2:0] state;
    logic[2:0] nextState;

    Registers register( clk, reset, nextState, state);

    NextStateLogic nsl( state, inputs, nextState);

    OutputLogic outLogic( state, la, lb);

endmodule

```

## NEXT STATE LOGIC (SYSTEM VERILOG)

```

module NextStateLogic( input logic[2:0] sin,
                    input logic[1:0] inputs,
                    output logic[2:0] sout);

    logic[31:0] decoderOut;
    logic[4:0] aa;

    assign aa = { sin[2], sin[1], sin[0], inputs[1], inputs[0]};

    Decoder dec( aa, decoderOut);

    assign sout[0] = decoderOut[0] || decoderOut[1] || decoderOut[8] || decoderOut[9] ||
                    decoderOut[10] || decoderOut[11] || decoderOut[16] || decoderOut[18] ||
                    decoderOut[24] || decoderOut[25] || decoderOut[26] || decoderOut[27];

    assign sout[1] = decoderOut[4] || decoderOut[5] || decoderOut[6] || decoderOut[7] ||
                    decoderOut[8] || decoderOut[9] || decoderOut[10] || decoderOut[11] ||
                    decoderOut[20] || decoderOut[21] || decoderOut[22] || decoderOut[23] ||
                    decoderOut[24] || decoderOut[25] || decoderOut[26] || decoderOut[27];

    assign sout[2] = decoderOut[12] || decoderOut[13] || decoderOut[14] || decoderOut[15] ||
                    decoderOut[16] || decoderOut[17] || decoderOut[18] || decoderOut[19] ||
                    decoderOut[20] || decoderOut[21] || decoderOut[22] || decoderOut[23] ||
                    decoderOut[24] || decoderOut[25] || decoderOut[26] || decoderOut[27];

endmodule

```

```
module Decoder( input logic[4:0] a,  
                output logic[31:0] out);  
  
    always_comb  
        case( a)  
            5'b00000:   out=32'b00000000000000000000000000000001;  
            5'b00001:   out=32'b00000000000000000000000000000010;  
            5'b00010:   out=32'b000000000000000000000000000000100;  
            5'b00011:   out=32'b0000000000000000000000000000001000;  
            5'b00100:   out=32'b00000000000000000000000000000010000;  
            5'b00101:   out=32'b000000000000000000000000000000100000;  
            5'b00110:   out=32'b0000000000000000000000000000001000000;  
            5'b00111:   out=32'b00000000000000000000000000000010000000;
```



[illegible]

endcase

endmodule

## REGISTERS (SYSTEM VERILOG)

```
module Registers( input logic clk, reset,
                  input logic[2:0] in,
                  output logic[2:0] out);

    always_ff@(posedge clk)
        if ( reset) out <= 3'b0;
        else        out <= in;

endmodule
```

# TRAFFIC LIGHTS TEST BENCH

```

module TrafficLightTB();

    logic clk, reset;

    logic[1:0] inputs;

    logic[1:0] la, lb, laExpected, lbExpected;

    logic [31:0] vectornum, errors;

    logic[5:0] testvectors[31:0];


    TrafficLights t( clk, reset, inputs, la, lb);


    //generate clock

    always
        begin
            clk = 1; #5;
            clk = 0; #5;
        end


    //load vectors

    initial
        begin
            $readmemb( "example.tv", testvectors);

            vectornum = 0; errors = 0;

            reset = 1; #5; reset = 0;

        end


    //apply test vector on rising edge of clock

    always @( posedge clk)
        begin
            #1; { inputs[1], inputs[0], laExpected[1], laExpected[0], lbExpected[1],
lbExpected[0]} = testvectors[vectornum];

            end


    //checking results on falling edge

    always @( negedge clk)
        begin
            if( ~reset) begin
                if((la[0] != laExpected[0]) || (la[1] != laExpected[1]) ||
                    (lb[0] != lbExpected[0]) || (lb[1] != lbExpected[1])) begin

                    $display( "Error: inputs = %b", {inputs[1], inputs[0]});
                end
            end
        end
    endmodule

```

```

        $display( " outputs: la = %b and lb = %b (expected: la = %b and lb = %b)",
{la[1], la[0]}, {lb[1], lb[0]}, {laExpected[1], laExpected[0]}, {lbExpected[1],
lbExpected[0]});

        errors = errors + 1;

    end

    if((la[0] === laExpected[0]) && (la[1] === laExpected[1]) &&
        (lb[0] === lbExpected[0]) && (lb[1] === lbExpected[1])) begin

        $display( "Worked: inputs = %b", {inputs[1], inputs[0]});

        $display( " outputs: la = %b and lb = %b (expected: la = %b and lb = %b)",
{la[1], la[0]}, {lb[1], lb[0]}, {laExpected[1], laExpected[0]}, {lbExpected[1],
lbExpected[0]});

    end

    vectornum = vectornum + 1;

    if( testvectors[ vectornum] === 6'bx) begin

        $display( "%d tests completed with %d errors", vectornum, errors);

        $finish;

    end

end

endmodule

```

## TRAFFIC LIGHTS TEST BENCH

```

set_property PACKAGE_PIN W5 [get_ports clk_in]
set_property IOSTANDARD LVCMOS33 [get_ports clk_in]
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports clk_in]

# Switches
set_property PACKAGE_PIN V17 [get_ports {inputs[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {inputs[1]}]
set_property PACKAGE_PIN V16 [get_ports {inputs[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {inputs[0]}]
set_property PACKAGE_PIN W16 [get_ports {reset}]
    set_property IOSTANDARD LVCMOS33 [get_ports {reset}]

# LEDs
set_property PACKAGE_PIN U16 [get_ports {la[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {la[0]}]
set_property PACKAGE_PIN E19 [get_ports {la[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {la[1]}]
set_property PACKAGE_PIN U19 [get_ports {la[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {la[2]}]

```

```
set_property PACKAGE_PIN V19 [get_ports {lb[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {lb[0]}]
set_property PACKAGE_PIN W18 [get_ports {lb[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {lb[1]}]
set_property PACKAGE_PIN U15 [get_ports {lb[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {lb[2]}]
```