

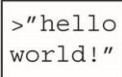


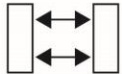
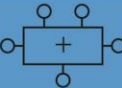
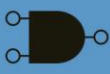
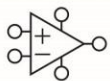


Chapter 4

Digital Design and Computer Architecture, 2nd Edition

David Money Harris and Sarah L. Harris

Chapter 4 :: Topics

- Introduction
- Combinational Logic
- Structural Modeling
- Sequential Logic
- More Combinational Logic
- Finite State Machines
- Parameterized Modules
- Testbenches

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

Introduction

- Hardware description language (HDL):
 - specifies logic function only
 - Computer-aided design (CAD) tool produces or *synthesizes* the optimized gates
- Most commercial designs built using HDLs
- Two leading HDLs:
 - **SystemVerilog**
 - developed in 1984 by Gateway Design Automation
 - IEEE standard (1364) in 1995
 - Extended in 2005 (IEEE STD 1800-2009)
 - **VHDL 2008**
 - Developed in 1981 by the Department of Defense
 - IEEE standard (1076) in 1987
 - Updated in 2008 (IEEE STD 1076-2008)



Introduction

- Manual simplification (truth tables-boolean equations) prone to errors (feasible only when the circuit is small)
- Higher level **abstraction** specifying the logical function
- CAD tool to produce **optimized** gates
- **Module**: a block of hardware with inputs and outputs. (good application of **modularity**)
- Major purposes of HDL is simulation and synthesis

Introduction

- HDL is a computer-based language that describes the digital hardware in a textual form
- Digital systems can be read by both humans and computers (exchange language between designers)
- Simulation is essential to test a system before it is built
- Modern design tools rely on HDL

HDL to Gates

- **Simulation**

- Inputs applied to circuit
- Outputs checked for correctness
- Millions of dollars saved by debugging in simulation instead of hardware

- **Synthesis**

- Transforms HDL code into a *netlist* describing the hardware (i.e., a list of gates and the wires connecting them)


IMPORTANT:

When using an HDL, think of the **hardware** the HDL should produce


HDL to Gates

$$f_1 = x_1x_2x_3' + x_1'x_2x_3$$

$$f_2 = x_1'x_2' + x_1x_2x_3$$

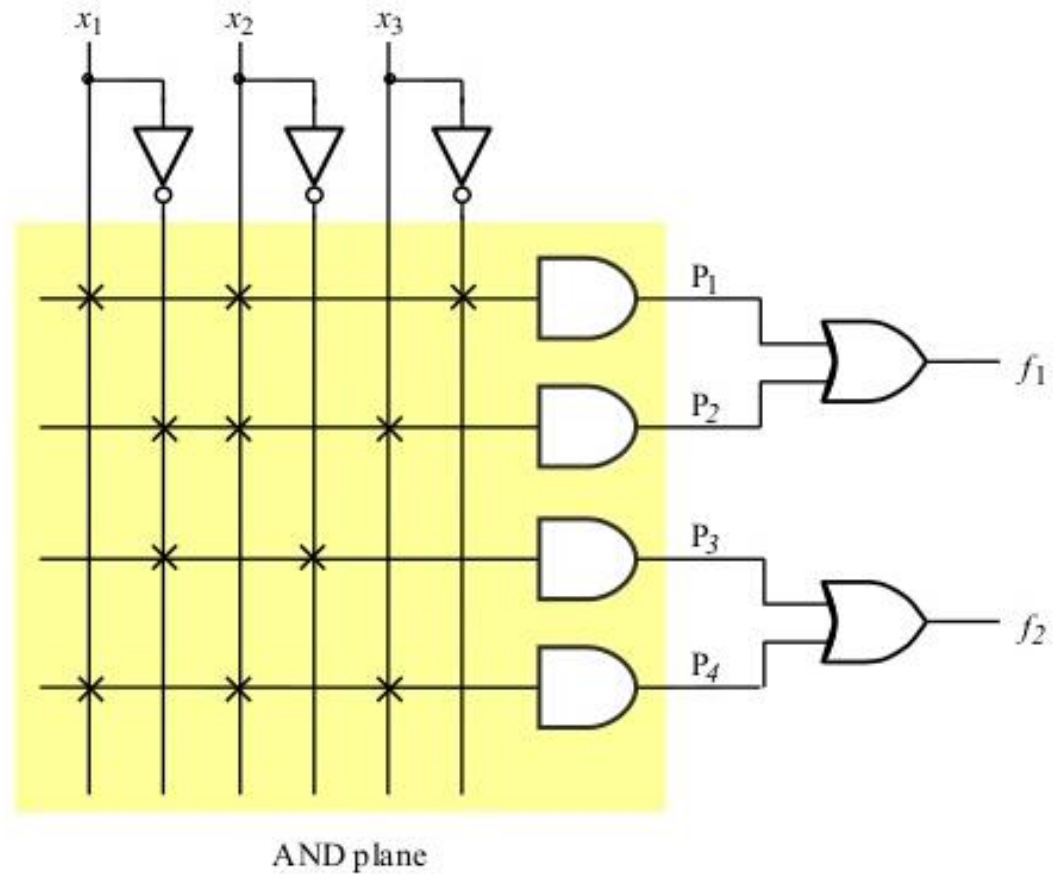

SystemVerilog Modules

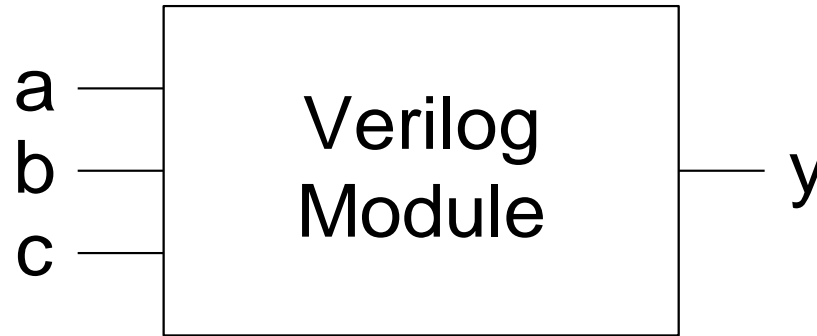

Two types of Modules:

- **Behavioral:** describe what a module does
- **Structural:** describe how it is built from simpler modules

Behavioral SystemVerilog

SystemVerilog:

```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```

Behavioral SystemVerilog

```
module example (input a, b, c,  
output y);
```

- Module name
- Listing of inputs and outputs

```
assign y = ~a & ~b & ~c |
```

```
a & ~b & ~c |
```

```
a & ~b & c;
```

- Input and output signals are boolean variables (0, 1, X, Z)

```
endmodule
```

- Assign describes combinational logic
- ~ = NOT
- & = AND
- |= OR

- Each row is terminated by a semicolon;

Structural SystemVerilog

```
module example(input logic a,b,c,  
               output logic y);  
  logic n1,n2in3,n4,n5,n6;
```

```
  inv  in1(n1,a);  
  inv  in1(n2,b);  
  inv  in1(n3,c);  
  and  a1(n4, n1,n2,n3);  
  and  a2(n5,a,n2,n3);  
  and  a3(n6,a,n2,c);  
  or   o1(y,n4,n5,n6);  
endmodule
```

- describing a module in terms of how it is **composed of simpler modules**


HDL Simulation

- ❑ Errors in hardware designs are called **bugs**. Eliminating the bugs from a digital system is important,
- ❑ Testing a system in the laboratory is **time-consuming**.
- ❑ Discovering the **cause of errors** in the lab can be extremely difficult,
- ❑ Only signals routed to the chip pins can be observed.
- ❑ Correcting errors after the system is built can be **expensive**.
- ❑ Logic **simulation** is essential to test a system before it is built.

HDL Simulation

SystemVerilog:

```
module example(input  logic a, b, c,
               output logic y);
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;
endmodule
```

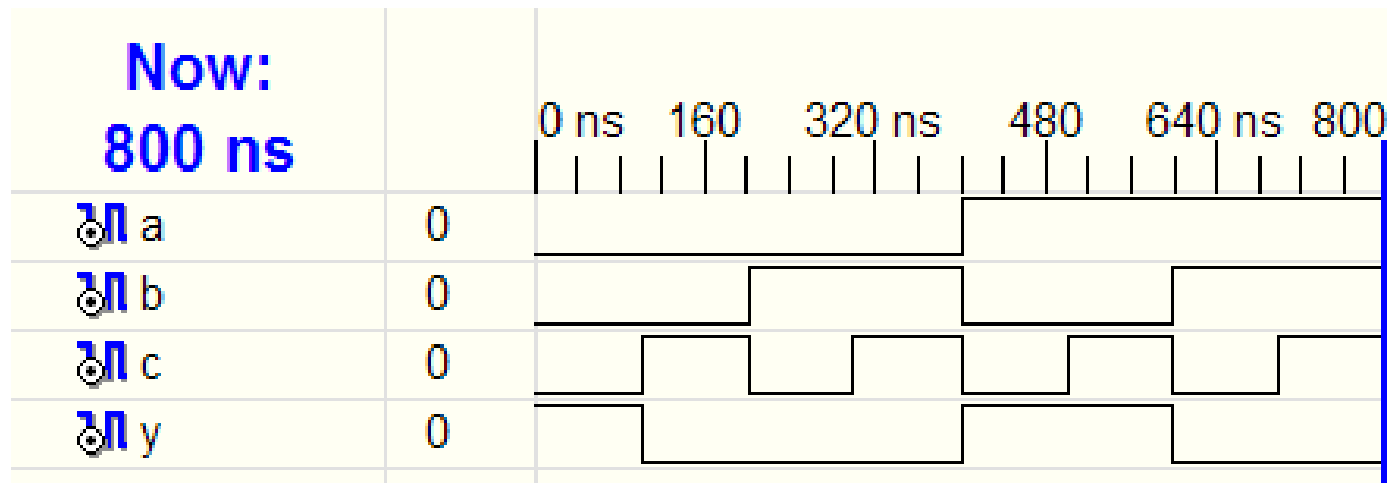

HDL Synthesis


- Synthesis transforms HDL code into a netlist **describing the hardware** (e.g., the logic gates and the wires connecting them).
- Synthesizer might perform **optimizations** to reduce the amount of hardware required.
- Netlist may be a text file, or it may be drawn as a schematic to help visualize the circuit.
- A command to print results on the screen during simulation does not translate into hardware.

HDL Synthesis

SystemVerilog:

```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```

Synthesis:

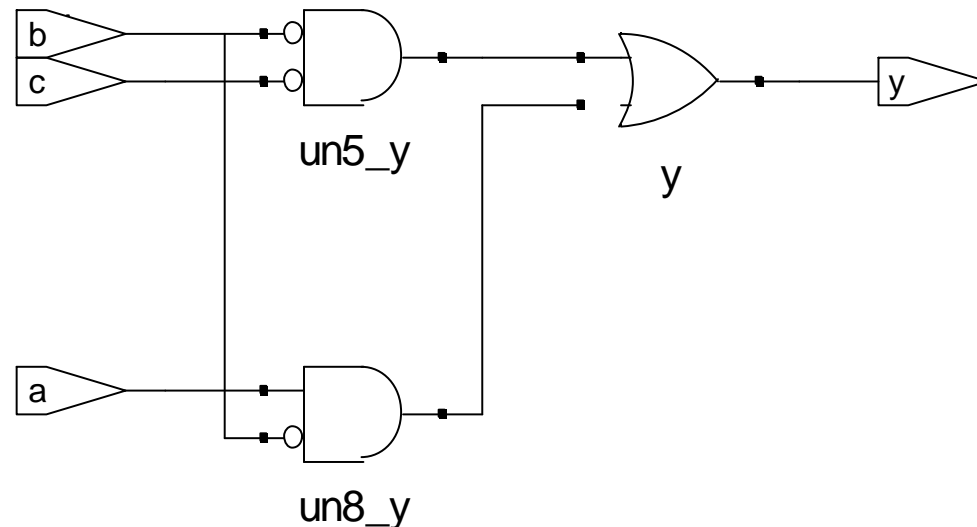

SystemVerilog Syntax

- Case sensitive
 - **Example:** `reset` and `Reset` are not the same signal.
- No names that start with numbers
 - **Example:** `2mux` is an invalid name
- Whitespace ignored
- Comments:
 - `//` single line comment
 - `/*` multiline
comment `*/`

Review₈

- Don't Cares
 - Floating: Z
 - Karnaugh Maps (K-Maps)
 - HDL (Simulation, Synthesis)
 - SystemVerilog Syntax
 - Operator Precedence
 - SystemVerilog Modules (Behavioral, Structural)
 - SystemVerilog Syntax
- 1st Midterm
14/11/2018
17:30

Structural Modeling - Hierarchy

```
module and3(input  logic a, b, c,  
            output logic y);  
    assign y = a & b & c;  
endmodule
```

```
module inv(input  logic a,  
            output logic y);  
    assign y = ~a;  
endmodule
```

```
module nand3(input  logic a, b, c  
             output logic y);  
    logic n1;                                // internal signal  
  
    and3 andgate(a, b, c, n1);              // instance of and3  
    inv  inverter(n1, y);                   // instance of inverter  
endmodule
```




Bitwise Operators

```

module gates(input  logic [3:0]  a, b,
              output logic [3:0] y1, y2, y3, y4, y5);
    /* Five different two-input logic
       gates acting on 4 bit busses */
    assign y1 = a & b;      // AND
    assign y2 = a | b;      // OR
    assign y3 = a ^ b;      // XOR
    assign y4 = ~(a & b);   // NAND
    assign y5 = ~(a | b);   // NOR
endmodule

```

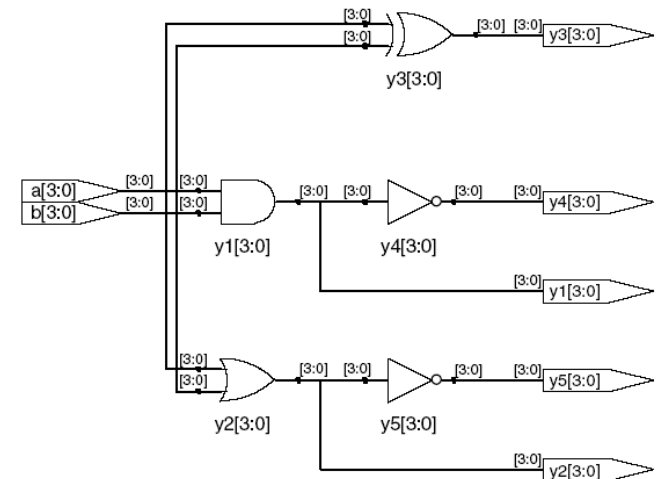// single line comment
 /*...*/ multiline comment




Bitwise Operators

- $a[3:0]$ – 4 bit bus ($a[3]..a[0]$ little endian order)
- $a[4:1]$ – 4 bit bus ($a[4]..a[1]$)
- $a[0:3]$ – 4 bit bus ($a[0]..a[3]$ big endian order)

Reduction Operators
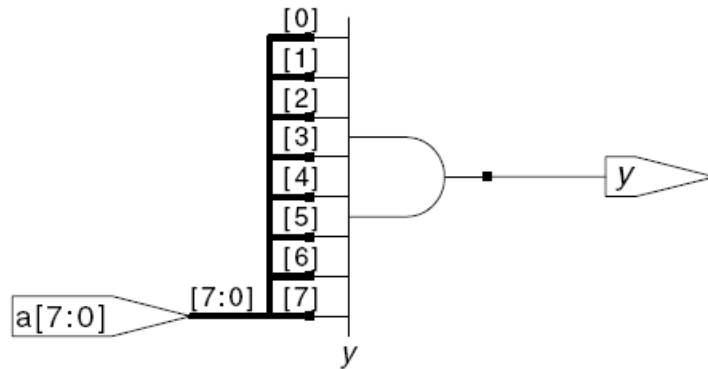
```
module and8(input  logic [7:0] a,  
            output logic      y);  
    assign y = &a;  
    // &a is much easier to write than  
    // assign y = a[7] & a[6] & a[5] & a[4] &  
    //               a[3] & a[2] & a[1] & a[0];  
endmodule
```




Reduction Operators

- Also $|$, $^$, $\sim\&$, and $\sim|$ reduction operators are available for OR, XOR, NAND, and NOR as well.
- Ex: A multi-input XOR performs parity, returning TRUE if an odd number of inputs are TRUE.

Conditional Assignment

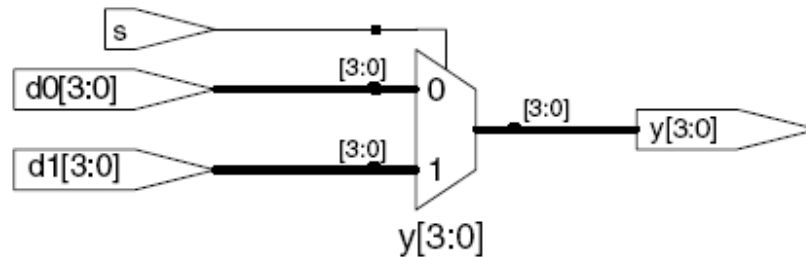
```
module mux2(input  logic [3:0] d0, d1,  
            input  logic      s,  
            output logic [3:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```



? : is also called a *ternary operator* because it operates on 3 inputs: s , $d1$, and $d0$.

Internal Variables

```
module fulladder(input  logic a, b, cin,  
                output logic s, cout);  
    logic p, g;    // internal nodes  
  
    assign p = a ^ b;  
    assign g = a & b;  
  
    assign s = p ^ cin;  
    assign cout = g | (p & cin);  
endmodule
```

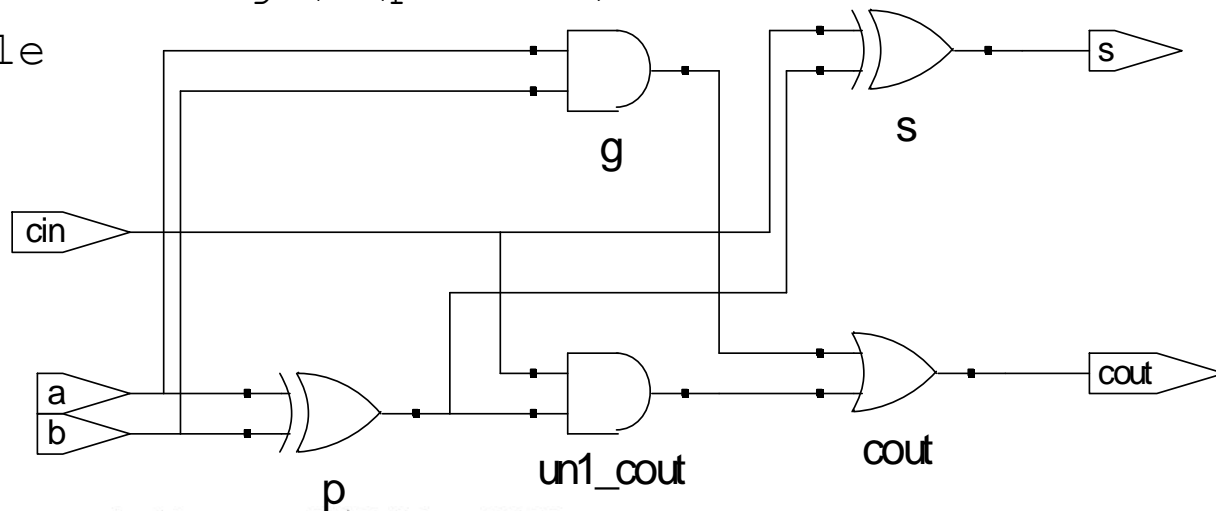

Precedence

Order of operations

Highest

\sim	NOT
$*, /, \%$	mult, div, mod
$+, -$	add, sub
$<<, >>$	shift
$<<<, >>>$	arithmetic shift
$<, <=, >, >=$	comparison
$==, !=$	equal, not equal
$\&, \sim \&$	AND, NAND
$\wedge, \sim \wedge$	XOR, XNOR
$, \sim $	OR, NOR
$?:$	ternary operator

Lowest

Numbers

Format: N'Bvalue

N = number of bits, **B** = base

N'B is optional but recommended (default is decimal)

Number	# Bits	Base	Decimal Equivalent	Stored
3'b101	3	binary	5	101
'b11	unsized	binary	3	00...0011
8'b11	8	binary	3	00000011
8'b1010_1011	8	binary	171	10101011
3'd6	3	decimal	6	110
6'o42	6	octal	34	100010
8'hAB	8	hexadecimal	171	10101011
42	Unsize	decimal	42	00...0101010



Bit Manipulations: Example 1

```
assign y = {a[2:1], {3{b[0]}}}, a[0], 6'b100_010};
```

```
// if y is a 12-bit signal, the above statement produces:
```

```
y = a[2] a[1] b[0] b[0] b[0] a[0] 1 0 0 0 1 0
```

```
// underscores (_) are used for formatting only to make  
it easier to read. SystemVerilog ignores them.
```

Bit Manipulations: Example 2


SystemVerilog:

```

module mux2_8(input  logic [7:0] d0, d1,
              input  logic      s,
              output logic [7:0] y);

    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);
endmodule


```

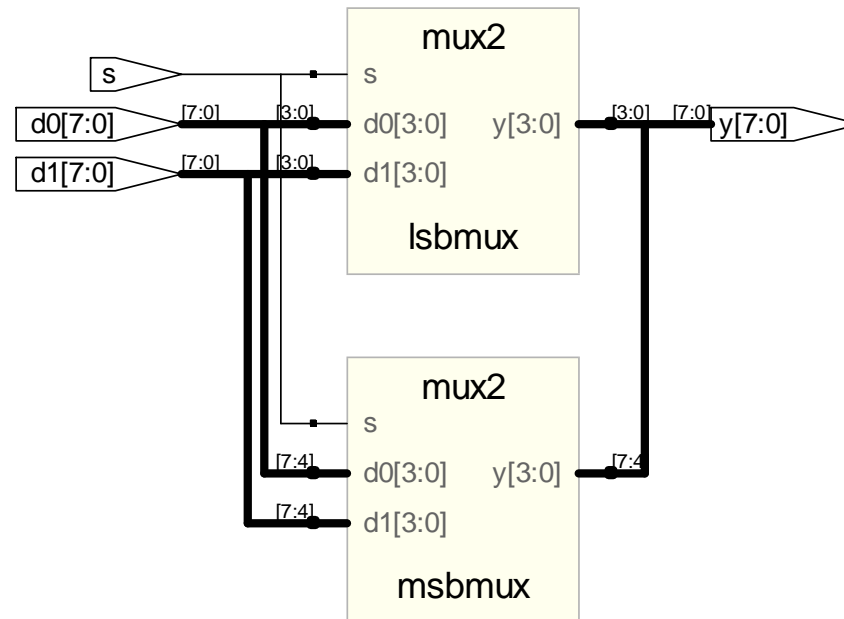

Z: Floating Output


SystemVerilog:
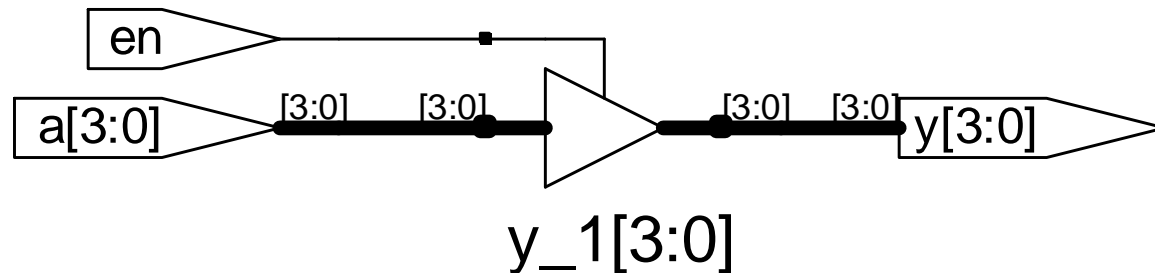
```
module tristate(input  logic [3:0] a,  
               input  logic      en,  
               output logic [3:0] y);  
    assign y = en ? a : 4'bz;  
endmodule
```



Delays

```
module example(input  logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} = ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

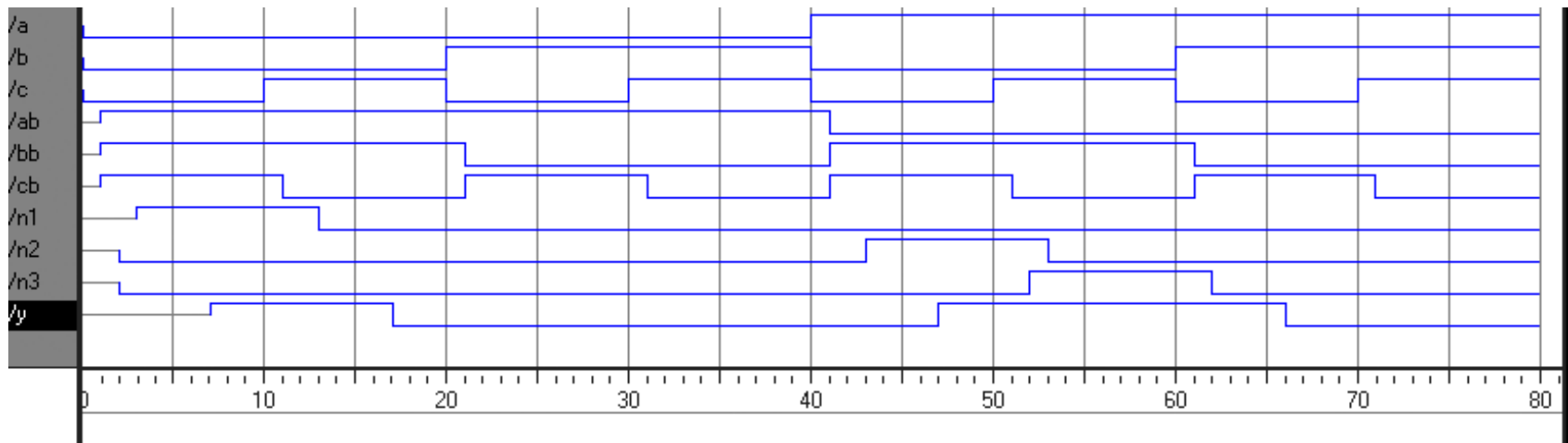


Delays

```

module example(input  logic a, b, c,
                output logic y);
    logic ab, bb, cb, n1, n2, n3;
    assign #1 {ab, bb, cb} =
                ~{a, b, c};
    assign #2 n1 = ab & bb & cb;
    assign #2 n2 = a & bb & cb;
    assign #2 n3 = a & bb & c;
    assign #4 y = n1 | n2 | n3;
endmodule

```

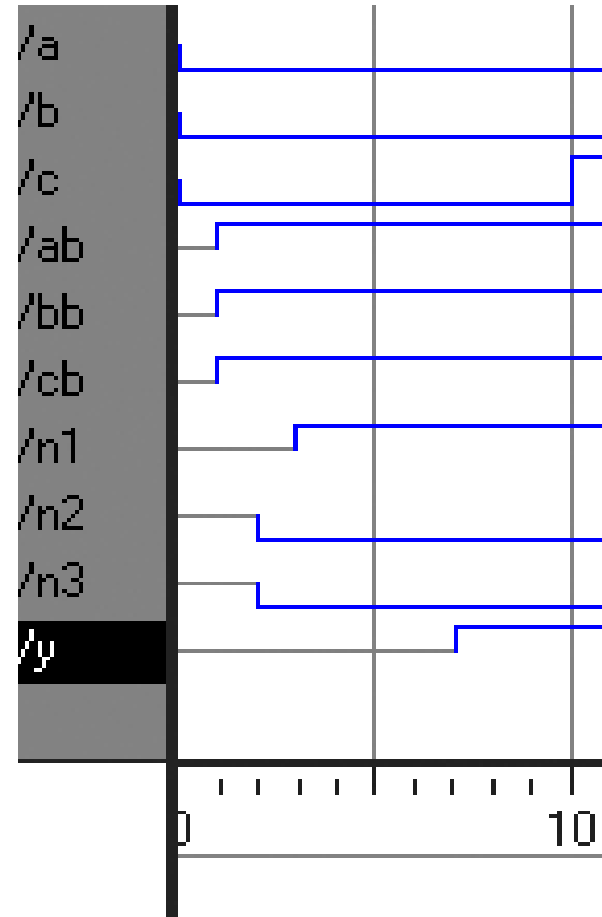

Parameterized Modules

2:1 mux:

```
module mux2
    #(parameter width = 8)    // name and default value
    (input  logic [width-1:0] d0, d1,
     input  logic              s,
     output logic [width-1:0] y);
    assign y = s ? d1 : d0;
endmodule
```

Instance with 8-bit bus width (uses default):

```
mux2 mux1(d0, d1, s, out);
```

Instance with 12-bit bus width:

```
mux2 #(12) lowmux(d0, d1, s, out);
```



Testbenches

- HDL that tests another module: *device under test* (dut)
- Not synthesizable
- Types:
 - Simple
 - Self-checking
 - Self-checking with testvectors

Testbench Example

- Write SystemVerilog code to implement the following function in hardware:

$$y = \overline{b}\overline{c} + a\overline{b}$$

- Name the module `sillyfunction`

Testbench Example

- Write SystemVerilog code to implement the following function in hardware:

$$y = \overline{b}\overline{c} + a\overline{b}$$

```
module sillyfunction(input  logic a, b, c,  
                    output logic y);  
    assign y = ~b & ~c | a & ~b;  
endmodule
```

Simple Testbench

```
module testbench1();  
    logic a, b, c;  
    logic y;  
    // instantiate device under test  
    sillyfunction dut(a, b, c, y);  
    // apply inputs one at a time  
    initial begin  
        a = 0; b = 0; c = 0; #10;  
        c = 1; #10;  
        b = 1; c = 0; #10;  
        c = 1; #10;  
        a = 1; b = 0; c = 0; #10;  
        c = 1; #10;  
        b = 1; c = 0; #10;  
        c = 1; #10;  
    end  
endmodule
```



Self-checking Testbench

```
module testbench2();  
    logic a, b, c;  
    logic y;  
    sillyfunction dut(a, b, c, y); // instantiate dut  
    initial begin // apply inputs, check results one at a time  
        a = 0; b = 0; c = 0; #10;  
        if (y !== 1) $display("000 failed.");  
        c = 1; #10;  
        if (y !== 0) $display("001 failed.");  
        b = 1; c = 0; #10;  
        if (y !== 0) $display("010 failed.");  
        c = 1; #10;  
        if (y !== 0) $display("011 failed.");  
        a = 1; b = 0; c = 0; #10;  
        if (y !== 1) $display("100 failed.");  
        c = 1; #10;  
        if (y !== 1) $display("101 failed.");  
        b = 1; c = 0; #10;  
        if (y !== 0) $display("110 failed.");  
        c = 1; #10;  
        if (y !== 0) $display("111 failed.");  
    end  
endmodule
```




Testbench with Testvectors

- Testvector file: inputs and expected outputs
- Testbench:
 1. Generate clock for assigning inputs, reading outputs
 2. Read testvectors file into array
 3. Assign inputs, expected outputs
 4. Compare outputs with expected outputs and report errors



Testbench with Testvectors

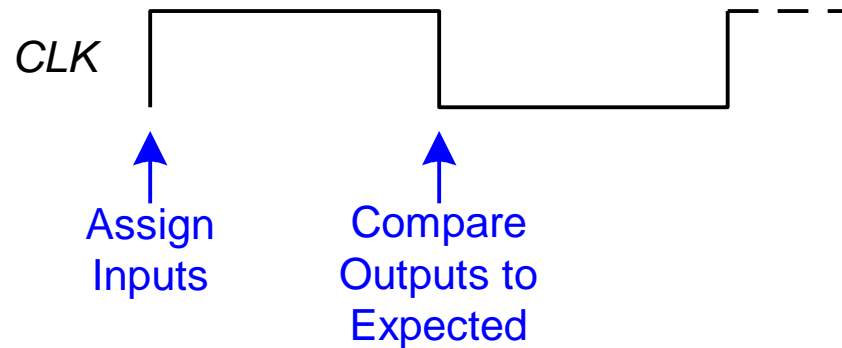- Testbench clock:
 - assign inputs (on rising edge)
 - compare outputs with expected outputs (on falling edge).



- Testbench clock also used as clock for synchronous sequential circuits

Testvectors File

- File: `example.tv`
- contains vectors of `abc_yexpected`

```
000_1
001_0
010_0
011_0
100_1
101_1
110_0
111_0
```


1. Generate Clock

```
module testbench3();  
    logic          clk, reset;  
    logic          a, b, c, yexpected;  
    logic          y;  
    logic [31:0] vectornum, errors;    // bookkeeping variables  
    logic [3:0] testvectors[10000:0]; // array of testvectors  
  
    // instantiate device under test  
    sillyfunction dut(a, b, c, y);  
  
    // generate clock  
    always          // no sensitivity list, so it always executes  
    begin  
        clk = 1; #5; clk = 0; #5;  
    end
```

2. Read Testvectors into Array

```
// at start of test, load vectors and pulse reset
```

```
initial
```

```
begin
```

```
    $readmemb("example.tv", testvectors);
```

```
    vectornum = 0; errors = 0;
```

```
    reset = 1; #27; reset = 0;
```

```
end
```

```
// Note: $readmembh reads testvector files written in
```

```
// hexadecimal
```

3. Assign Inputs & Expected Outputs

```
// apply test vectors on rising edge of clk
always @(posedge clk)
begin
    #1; {a, b, c, yexpected} = testvectors[vectornum];
end
```

4. Compare with Expected Outputs

```
// check results on falling edge of clk
always @(negedge clk)
  if (~reset) begin // skip during reset
    if (y !== yexpected) begin
      $display("Error: inputs = %b", {a, b, c});
      $display("  outputs = %b (%b expected)", y, yexpected);
      errors = errors + 1;
    end
  end

// Note: to print in hexadecimal, use %h. For example,
//      $display("Error: inputs = %h", {a, b, c});
```

4. Compare with Expected Outputs

```
// increment array index and read next testvector
    vectornum = vectornum + 1;
    if (testvectors[vectornum] === 4'bx) begin
        $display("%d tests completed with %d errors",
            vectornum, errors);
        $finish;
    end
end
endmodule
```

// `===` and `!==` can compare values that are 1, 0, x, or z.

Waveout *example*

